

UNIVERSITY OF ABUJA
PHYSICS DEPARTMENT
PHY 204 TEST

- Q1(a) Two concentric metal spheres of radii x and y ($x > y$) have the larger sphere earthed. Drive an expression for the capacitance of the system.
- (b) Three concentric metal spheres have radii 10cm , 20cm , 30cm . The outer sphere is earthed whilst the inner one is charged to a potential of 1000V , the intermediate sphere being isolated and uncharged. Find the charge on this inner sphere.

PHY 204 Test Solutions

$$(4\pi\epsilon_0)^{-1} = 9 \times 10^9 \text{ Nm}^2/\text{C}^2$$

(a)

$$V = V_+ + V_-$$

$$= \frac{q}{4\pi\epsilon_0 y} - \frac{q}{4\pi\epsilon_0 x}$$

$$4\pi\epsilon_0 = \frac{1}{9 \times 10^9}$$

$$= \frac{q}{4\pi\epsilon_0} \left\{ \frac{1}{y} - \frac{1}{x} \right\}$$

$$= \frac{q}{4\pi\epsilon_0} \left\{ \frac{x-y}{yx} \right\}$$

$$C = \frac{q}{V} = \frac{4\pi\epsilon_0 yx}{x-y}$$

(b)

$$C = \frac{4\pi\epsilon_0 (0.1 \times 0.3)}{(0.3 - 0.1)}$$

$$= \frac{0.03 \cdot 4\pi\epsilon_0}{0.2}$$

$$\therefore \frac{q}{V} = \frac{0.03 \cdot 4\pi\epsilon_0}{0.2}$$

$$q = \frac{0.03 \cdot 4\pi\epsilon_0}{0.2} \times V$$

$$= 1.668 \times 10^{-8} C$$

PHY 204

SOLUTION TO ASSIGNMENT 1

I. At node V_1

$$7 - 3V_1 - 5 - 1(V_1 - V_2) = 0$$

$$4V_1 - V_2 = 2 \quad \text{--- (1)}$$

At node V_2

$$5 + (V_1 - V_2) - 3V_2 - 2(V_2 - V_3) = 0$$

$$-V_1 + 6V_2 - 2V_3 = 5 \quad \text{--- (2)}$$

At Node V_3

$$2(V_2 - V_3) + 17 - V_3 - 4V_3 = 0$$

$$-2V_2 + 7V_3 = 17 \quad \text{--- (3)}$$

These equations may be solved for the node voltages using one of the variety of methods for simultaneous equations to form eqn (1)

$$V_1 = \frac{V_2 + 2}{4} \quad \text{--- (4)}$$

Substituting for V_1 in (2) we have

$$-\left(\frac{V_2 + 2}{4}\right) + 6V_2 - 2V_3 = 5$$

$$-\frac{V_2}{4} - \frac{1}{2} + 6V_2 - 2V_3 = 5$$

$$\frac{23}{4}V_2 - 2V_3 = 5\frac{1}{2} \quad \text{--- (5)}$$

Solving (5) and (3) simultaneously, we have

$$-2V_2 + 7V_3 = 17 \quad \times 2$$

$$\frac{23}{4}V_2 - 2V_3 = 5\frac{1}{2} \quad \times 7$$

$$-4V_2 + 14V_3 = 34 \quad (6)$$

$$\frac{161}{4}V_2 - 14V_3 = 77\frac{1}{2} \quad (7)$$

(6) + (7) gives

$$36\frac{1}{4}V_2 + 72\frac{1}{2}$$

$$V_2 = 2V$$

Substituting (8) into (4) we have

$$V_1 = \frac{V_2 + 2}{4} = 1V$$

V_3 also yields from (3)

$$-4 + 7V_3 = 17$$

$$V_3 = 3V$$

Assignment II

At mesh I

$$-V_{g_1} + R_1 i_1 + R_2 (i_1 - i_2) + R_3 (i_1 - i_3) = 0$$

$$(R_1 + R_2 + R_3) i_1 - R_2 i_2 - R_3 i_3 = V_{g_1}$$

At mesh II

$$i_2 R_4 + V_{g_2} + R_5 (i_2 - i_3) + R_2 (i_2 - i_1) = 0$$

$$(R_2 + R_4 + R_5) i_2 - R_2 i_1 - R_5 i_3 = -V_{g_2}$$


At mesh III

$$i_3 R_6 - V_{g_1} + R_3 (i_3 - i_1) + R_5 (i_3 - i_2) = 0$$

$$(R_3 + R_5 + R_6) i_3 - R_3 i_1 - R_5 i_2 = V_{g_1}$$

Assignment II

RL Parallel

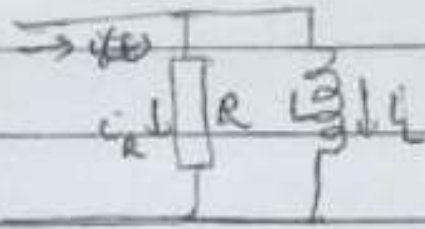

$$V = V_m \cos \omega t$$

$$i_T = i_R + i_L$$

$$= \frac{V}{R} + \frac{1}{L} \int V dt$$

$$= \frac{V_m \cos \omega t}{R} + \frac{V_m \sin \omega t}{\omega L}$$

$$\therefore i_T = A \cos(\omega t - \phi)$$

where

$$A = V_m \sqrt{\frac{1}{R^2} + \left(\frac{1}{\omega L}\right)^2}$$

$$\phi = \tan^{-1} \frac{R}{\omega L}$$

R-C Parallel

$$V = V_m \sin \omega t$$

$$i_T = i_R + i_C$$

$$= \frac{V}{R} + C \frac{dV}{dt}$$


$$= \frac{V_m \sin \omega t}{R} + \omega C V_m \cos \omega t$$

$$= A \sin(\omega t + \beta)$$

$$A = \sqrt{\frac{1}{R^2} + (\omega C)^2} V_m$$

$$\beta = \tan^{-1} \omega C R$$

R-C-L Parallel

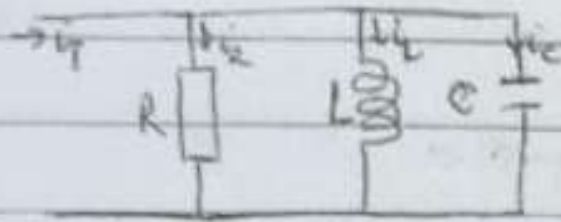

$$v_s = \sqrt{2} V_m \sin \omega t$$

$$i_T = i_R + i_L + i_C$$

$$= \frac{v}{R} + \frac{1}{L} \int v dt + C \frac{dv}{dt}$$

$$i_T = \frac{V_m \sin \omega t}{R} - \frac{V_m \cos \omega t}{\omega L} + \omega C V_m \cos \omega t$$


$$i_T = A \sin(\omega t + \phi)$$

where

$$A = \sqrt{\frac{1}{R^2} + \left(\omega C - \frac{1}{\omega L}\right)^2} V_m$$

$$\phi = \tan^{-1} \frac{\left(\omega C - \frac{1}{\omega L}\right)}{R}$$

ASSUMPTION (ii)

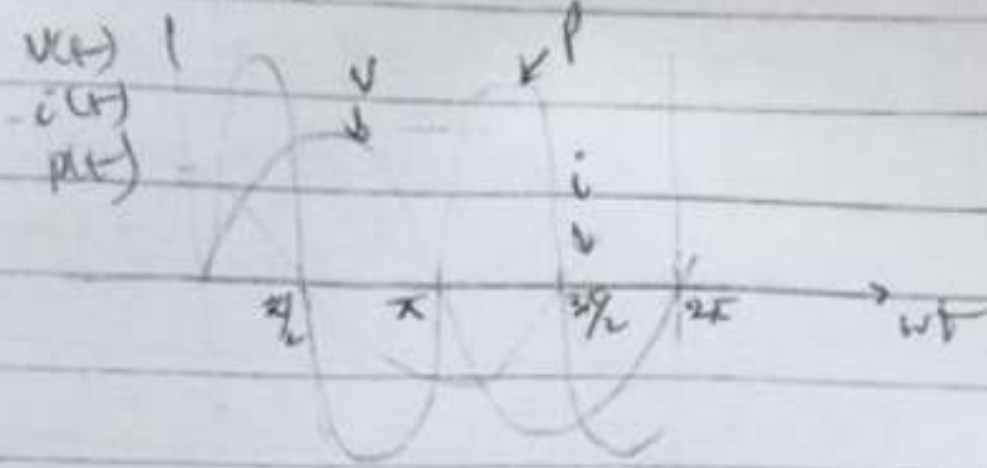

PURE CAPACITOR

Here i leads v by $\pi/2$

Pure Resistor

Consider a pure resistor with

$$v = V_m \sin \omega t$$


$$i = I_m \sin \omega t$$

Here v & i are in phase

$$p = vi = V_m I_m \sin^2 \omega t$$

$$\sin^2 \omega t = \frac{1}{2}(1 - \cos 2\omega t)$$
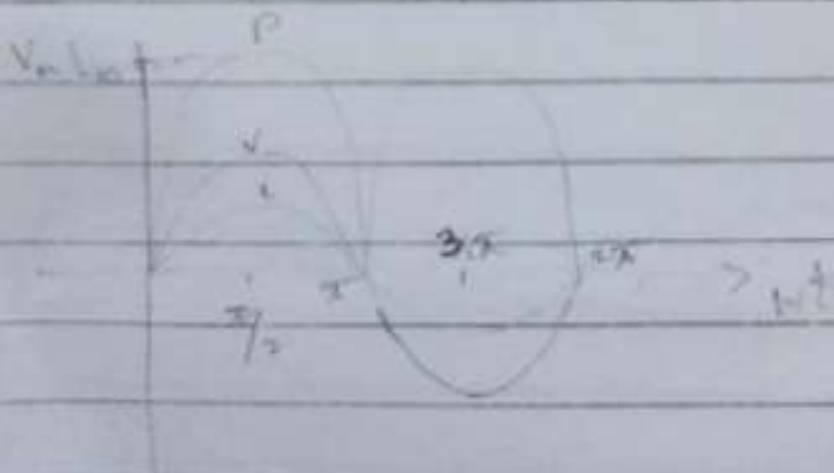
$$\therefore p = \frac{1}{2} V_m I_m (1 - \cos 2\omega t)$$



p has twice the frequency of v or i

p always varies from zero to a maximum value of $V_m I_m$

The average value of p over the entire cycle is

$$\frac{1}{2} V_m I_m$$

Generally when $v = V_m \sin \omega t$ is applied to a network, the resulting current is $i = I_m \sin(\omega t + \theta)$

The phase angle θ can be positive (i.e. Capacitor) or negative (inductive).

$$P = V_m I_m \sin \omega t \sin(\omega t + \theta)$$

$$\sin A \sin B = \frac{1}{2} \left\{ \cos(A-B) - \cos(A+B) \right\}$$

$$\cos -A = \cos A$$

$$\therefore P = \frac{1}{2} V_m I_m \left\{ \cos \theta - \cos(2\omega t + \theta) \right\}$$

P consists of a sinusoidal term $-\frac{1}{2} V_m I_m \cos(2\omega t + \theta)$ which have an average power value of zero and a constant term $\frac{1}{2} V_m I_m \cos \theta$